

Homework 5

CDA3103: Digital Logic and Computer Organization

Due Friday, March 8, 2019 (11:59 PM)

1. (40 point) Design a single-bit ALU, an 8-bit ALU and a 8 by 8 multiplier

- Design a single-bit ALU in Logisim and add it as subcircuit to Logisim. Name it **1-bit ALU**. (It's block diagram is available in your lecture notes.)
- Design a 8-bit ALU using 8 single-bit ALUs designed in part A and add it as subcircuit to Logisim (name it **8-bit ALU**).
- Design a multiplier version 3 (discussed in the class) using an 8-bit ALU and add it as subcircuit to Logisim. Name it "**multiplier_8.8**".
- On the main page use the multiplier designed in part C to multiply two 8-bit unsigned integers, A and B. The product should be displayed using hex-displays.

Note: you are not allowed to use built-in multiplier. But using the other built-in gates in the Logisim is allowed.

At the end, submit just one single **Yourname_HW5.circ** file including all of subcircuits and circuits above. (In the following figure, a decimal probe has been used to show the product value, but you should use Hex-display.)

